

### Introduction


The ST2S06 is a dual synchronous step-down DC-DC converter optimized for powering low-voltage digital cores in ODD applications and, generally, used to replace the high current linear solution when the power dissipation may cause a high heating of the application environment. It provides up to 0.5 A over an input voltage range of 2.5 V to 5.5 V.

A high switching frequency (1.5 MHz) allows the use of tiny surface-mount components. A resistor divider to set the output voltage value, an inductor and two capacitors are required for every channel. In addition, a low output ripple is guaranteed by the current mode PWM topology and by the use of low ESR surface-mount ceramic capacitors.

The device is thermal protected and current limited to prevent damage due to accidental short-circuit.

The family is available in the QFN12L (4x4 mm) package.

**Figure 1. ST2S06 - simplified schematic**

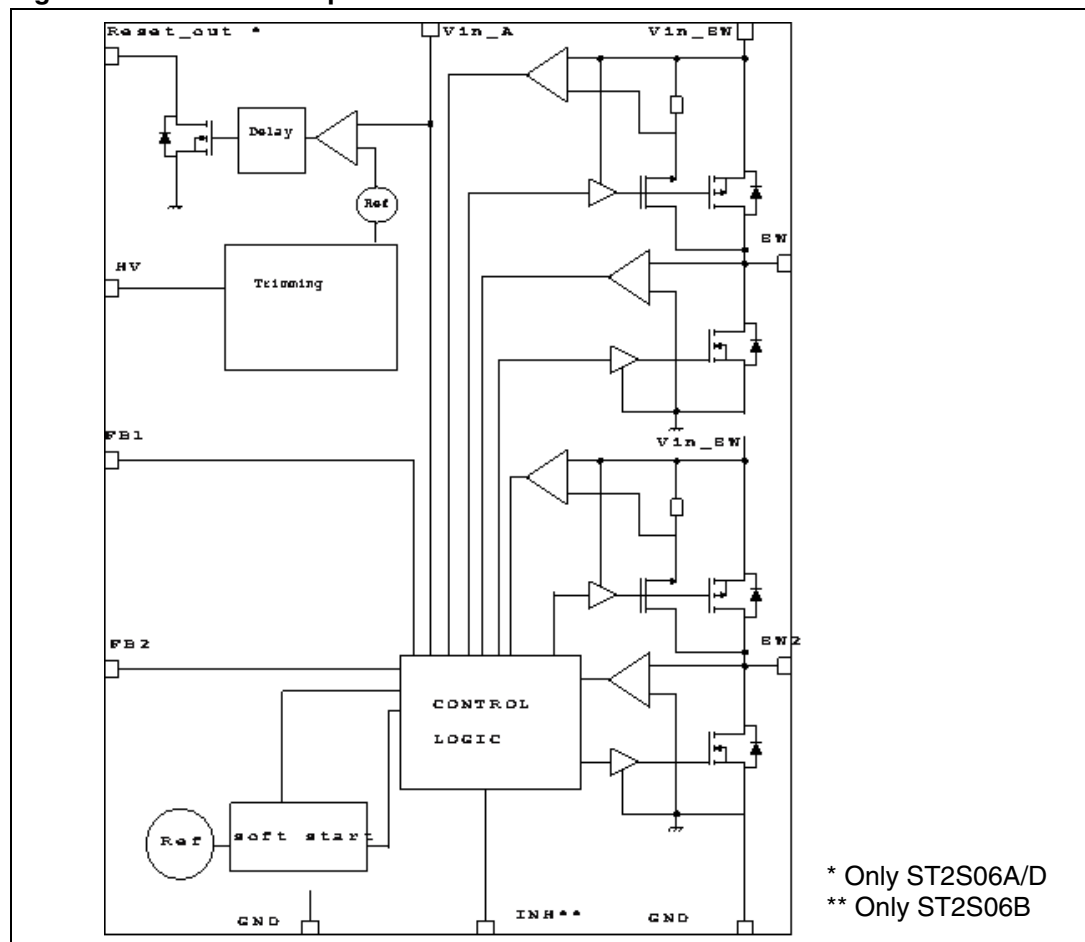

# Contents

- 1      ST2S06 description ..... 4**
  - 1.1    Inhibit function (ST2S06B only) ..... 7
  - 1.2    Reset function (ST2S06A and ST2S06D only) ..... 7
  - 1.3    Short-circuit protection ..... 10
  
- 2      Selecting components for applications ..... 11**
  - 2.1    Output voltage selection ..... 11
  - 2.2    Input capacitor ..... 12
  - 2.3    Output capacitor ..... 13
  - 2.4    Inductor ..... 13
  - 2.5    Layout considerations ..... 14
  
- 3      Thermal considerations ..... 15**
  
- 4      Demonstration board usage recommendation ..... 16**
  - 4.1    External component selection ..... 18
    - 4.1.1    Capacitors selection ..... 19
    - 4.1.2    Inductor selection ..... 19
  
- 5      Bill of materials ..... 21**
  
- 6      Recommended footprint ..... 22**
  
- 7      Revision history ..... 22**

## List of figures

Figure 1.	ST2S06 - simplified schematic . . . . .	1
Figure 2.	Inductor current at light load . . . . .	4
Figure 3.	Output voltage ripple at light load . . . . .	5
Figure 4.	Inductor current in PWM . . . . .	5
Figure 5.	Output voltage ripple in PWM . . . . .	6
Figure 6.	Inrush current . . . . .	6
Figure 7.	ST2S06B - inhibit voltage vs. temperature . . . . .	7
Figure 8.	ST2S06A\D - reset block diagram . . . . .	8
Figure 9.	ST2S06A\D - reset function . . . . .	8
Figure 10.	Pull-up resistor . . . . .	9
Figure 11.	ST2S06D - delay time . . . . .	9
Figure 12.	Reset_in threshold vs. temperature . . . . .	9
Figure 13.	TDEL vs. temperature . . . . .	10
Figure 14.	Typical application schematic . . . . .	11
Figure 15.	Feedback voltage vs. temperature . . . . .	12
Figure 16.	Layout considerations . . . . .	14
Figure 17.	Demonstration board layout . . . . .	16
Figure 18.	Demonstration board - top layer . . . . .	17
Figure 19.	Demonstration board - bottom layer . . . . .	17
Figure 20.	Demonstration board schematic for ST2S06A\D . . . . .	18
Figure 21.	Demonstration board schematic for ST2S06B . . . . .	18
Figure 22.	Efficiency vs. output current . . . . .	19
Figure 23.	Efficiency vs. inductor . . . . .	20
Figure 24.	Efficiency vs. output voltage . . . . .	20
Figure 25.	QFN12L (4x4 mm) footprint recommended data . . . . .	22

# 1 ST2S06 description


The ST2S06 is a dual adjustable current mode PWM synchronous step-down DC/DC converter with an internal 0.5 A power switch. It is a complete 0.5 A dual switching regulator with internal compensation that eliminates the need for additional components.

The device is available in three versions, the ST2S06A and ST2S06D with a reset function and the ST2S06B with an inhibit function.


The ST2S06 family operates with typically 1.5 MHz fixed frequency.

To maintain good efficiency at both channels, the devices operate in power-save mode at light load (*Figure 2* and *3*). When the load increases it automatically switches to PWM (pulse width modulation) mode in order to reduce the output voltage ripple (*Figure 4* and *5*).

**Figure 2. Inductor current at light load**

 

**Figure 3. Output voltage ripple at light load**

 

**Figure 4. Inductor current in PWM**



 


Figure 5. Output voltage ripple in PWM

 

To clamp the error amplifier reference voltage, a Soft Start control block generating a voltage ramp is implemented. When switching on the power supply, it allows controlling the inrush current value.

Figure 6. Inrush current

 

Other protection circuits in the device are the thermal shutdown block which turns off the regulator when the junction temperature exceeds 150 °C (typ.) and the cycle-by-cycle current limiting that provides protection against shorted outputs.

Operation of the device requires few components: two inductors, three capacitors and two resistor dividers. The inductors chosen must be capable of not saturating at the peak current level. The value of the inductors should be selected keeping in mind that a large inductor value increases the efficiency at low output current and reduces output voltage ripple, while

a smaller inductor can be chosen when it is important to reduce the package size and the total application cost.

Finally, the ST2S06 family has been designed to work properly with X5R or X7R SMD ceramic capacitors both at input and at output. These capacitors, thanks to their very low series resistance (ESR), minimize the output voltage ripple. Other low ESR capacitors can be used according to the need of the application without compromising the correct functioning of the device.

Due to the high switching frequency and peak current, it is important to optimize the application environment by reducing the length of the PCB traces and placing all external components near the device.


## 1.1 Inhibit function (ST2S06B only)

The ST2S06B features an Inhibit function (pin 10). When the Inh voltage is higher than 1.3 V the device is On and if it is lower than 0.4 V the device is OFF. In shutdown mode consumption is lower than 1  $\mu$ A.

The Inh pin does not have an internal pull-up which means that you cannot leave the inhibit floating.

If the inhibit function is not used, the Inh pin must be connected to  $V_{in}$ .

**Figure 7. ST2S06B - inhibit voltage vs. temperature**

 

## 1.2 Reset function (ST2S06A and ST2S06D only)

Most ODD applications require a flag showing that the input voltage is in the correct range.

**Figure 8. ST2S06A/D - reset block diagram**


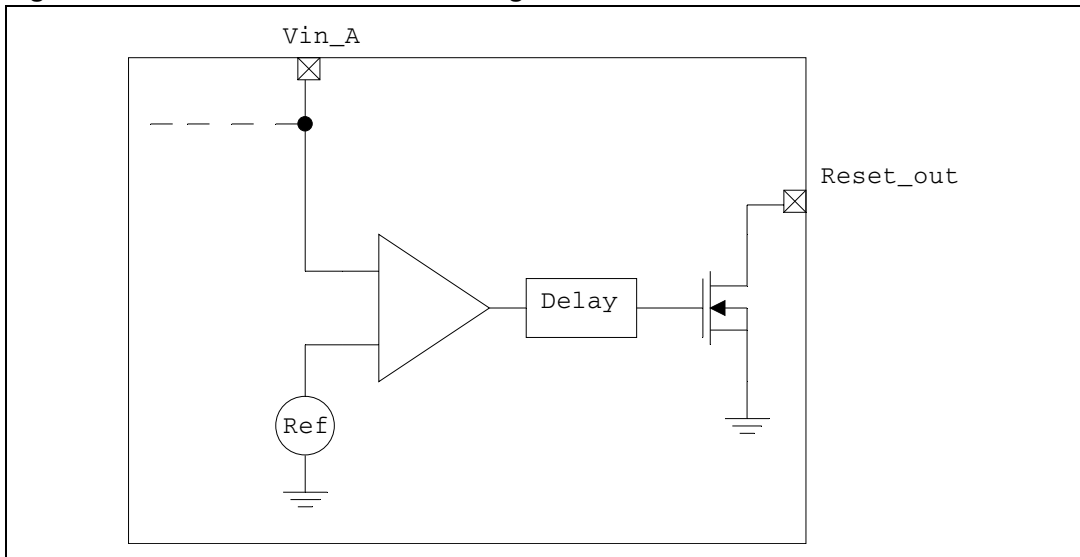


Figure 8 shows the simplified reset block diagram. A comparator senses the input voltage. When it is higher than  $V_{TL}$  (4.2 V for ST2S06A or 3.7 V for ST2S06D), the  $reset\_out$  pin goes to high impedance. If it is below  $V_{TH}$  (4.6 V for ST2S06A or 4.55 V max for ST2S06D), the  $reset\_out$  pin goes to low impedance with a delay of 100 ms (typ.) for ST2S06A or 65 ms (typ.) for ST2S06D (see Figure 9 and 11).

**Figure 9. ST2S06A/D - reset function**

 

The use of the Reset function requires an external pull-up resistor which must be connected between  $reset\_out$  pin and  $V_{in}$  or  $V_{out}$ . We suggest using a pull-up resistor for reset in the range of 100 k $\Omega$  to 1 M $\Omega$ . If the reset function is not used, the  $reset\_out$  pin must remain floating on the board.

In the application board (Figure 10),  $R_{pi}$  is used to pull up the  $reset\_out$  pin to  $V_{in}$  and  $R_{po}$  to pull up the  $reset\_out$  pin to  $V_{out1}$ . Of course the  $reset\_out$  pin can be connected only to  $V_{in}$  or  $V_{out}$ .



Figure 10. Pull-up resistor

 


Figure 11. ST2S06D - delay time

 


Figure 12. Reset\_in threshold vs. temperature


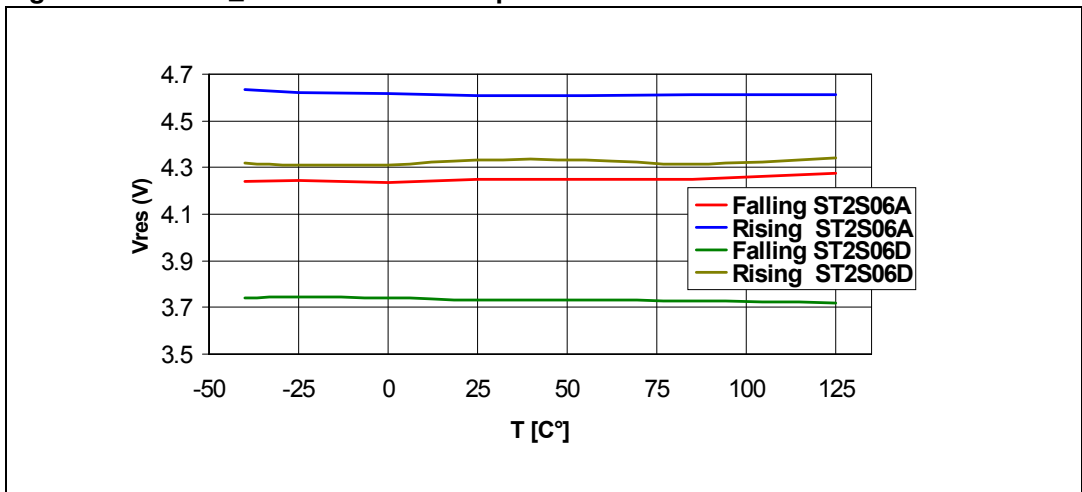


Figure 13.  $T_{DEL}$  vs. temperature

 

### 1.3 Short-circuit protection

In overcurrent protection mode, when the peak current reaches the current limit, the device reduces  $T_{on}$  to its minimum value. In these conditions, the duty cycle is strongly reduced and, in most of the applications, this is enough to limit the current to  $I_{lim}$ .

In case of heavy short-circuit at the output ( $V_{out}=0$  V) and depending on the application conditions ( $V_{in}$  value and parasitic effect of external components), the current peak could reach values higher than  $I_{lim}$ . This can be understood considering the inductor current ripple during the ON and OFF phases:

**Equation 1**

$$\text{ON phase} \quad \Delta I_L = \frac{(V_{in} - V_{out} - DCR_L \cdot I)}{L} \cdot T_{on}$$

**Equation 2**

$$\text{OFF phase} \quad \Delta I_L = \frac{(V_D + V_{out} + DCR_L \cdot I)}{L} \cdot T_{off}$$


Where  $V_D$  is the voltage drop across the internal NMOS and  $DCR_L$  is the series resistance of the inductor. In short-circuit conditions  $V_{out}$  is negligible. So, during  $T_{off}$ , the voltage applied to the inductor is very small and it can be that the current ripple in this phase does not compensate for the current ripple during  $T_{on}$ . The maximum current peak can be easily measured through the inductor with  $V_{out} = 0$  V (short-circuit) and  $V_{in}=V_{inmax}$ . In case the application has to sustain the short-circuit condition for a long time, the external components (mainly inductor) must be selected based on this value.

## 2 Selecting components for applications

This section provides information to assist in the selection of the most appropriate components for your applications.

Figure 14 shows the typical application schematic.

Figure 14. Typical application schematic

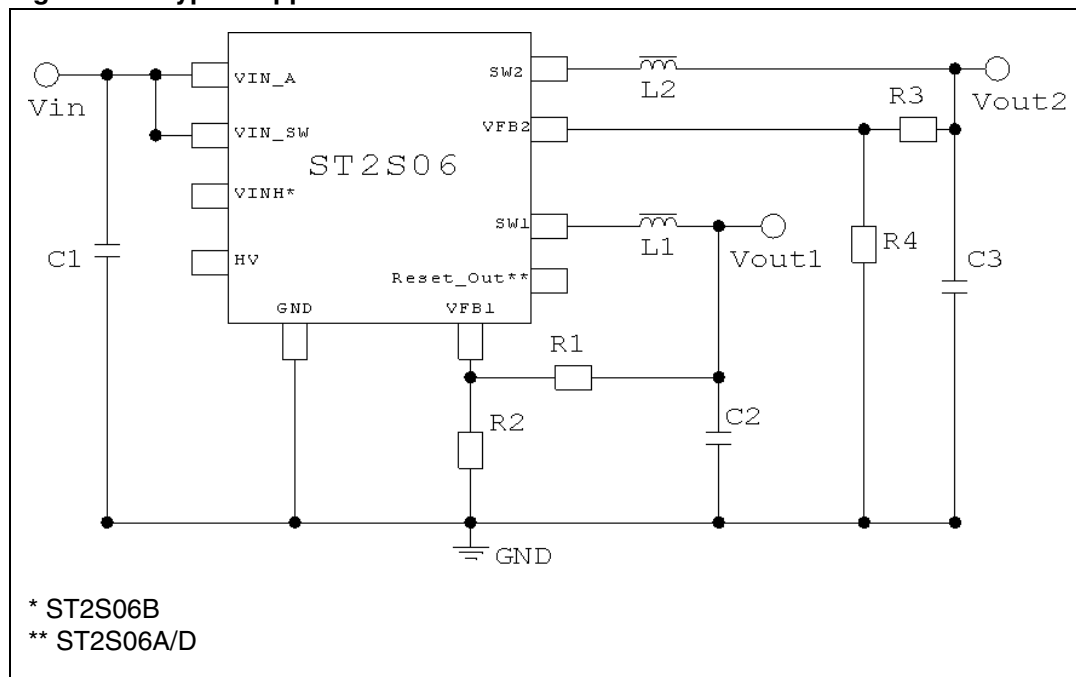

### 2.1 Output voltage selection

The output voltage can be adjusted from 0.8 V up to 85% of input voltage value by connecting a resistor divider between the output and the V<sub>FB</sub> pin.

You must choose the resistor divider according to the following equation:

Equation 3

$$V_{out} = V_{FB} \left[ 1 + \frac{R_1}{R_2} \right] \text{ with } V_{FB}=0.8 \text{ V}$$

Figure 13 shows the feedback voltage versus temperature.

We suggest using a resistor with a value in the range of 10 kΩ to 50 kΩ. Lower values are suitable as well, but will increase current consumption. Be aware that the duty cycle must be kept below 85% at all application conditions, so that:


Equation 4

$$D_{MAX} = \frac{V_{out} + V_F}{V_{inMIN} - V_{SW}} < 0.85$$

where V<sub>F</sub> is the voltage drop across the internal NMOS, and V<sub>SW</sub> represents the voltage drop across the internal PMOS.

For output voltages close to the feedback voltage, we suggest adding a very small capacitor in parallel to R1 in the range of 10 pF. Or, as an alternative, we suggest increasing the current in the resistor divider by decreasing the R1 and R2 value.

**Figure 15. Feedback voltage vs. temperature**

 

## 2.2 Input capacitor

The input capacitor must be able to support the maximum input operating voltage and the maximum RMS input current.

Since step-down converters draw current from the input impulses, the input current is squared and the height of each pulse is equal to the output current. The input capacitor has to absorb all this switching current that can be up to one half of the load current (worst case, with duty cycle of 50%).

For this reason, the quality of these capacitors has to be very high to minimize its power dissipation generated by the internal ESR, thus improving the system reliability and efficiency.

The critical parameter is usually the RMS current rating, which must be higher than the RMS input current. The maximum RMS input current (flowing through the input capacitor) is:

**Equation 5**

$$I_{RMS} = I_{out} \cdot \sqrt{D - \frac{2 \cdot D^2}{\eta} + \frac{D^2}{\eta}}$$

Where  $\eta$  is the expected system efficiency, D is the duty cycle, and  $I_{out}$  the output DC current. This function reaches its maximum value at  $D = 0.5$  and the equivalent RMS current is equal to  $I_{out}$  divided by 2 (considering  $\eta = 1$ ).

The maximum and minimum duty cycles are:

**Equation 6**

$$D_{MAX} = \frac{V_{out} + V_F}{V_{inMIN} - V_{SW}}$$

**Equation 7**

$$D_{\text{MIN}} = \frac{V_{\text{out}} + V_F}{V_{\text{inMAX}} - V_{\text{SW}}}$$

Where  $V_F$  it is the voltage drop across the internal NMOS and  $V_{\text{SW}}$  the voltage drop across the internal PMOS. Considering the range  $D_{\text{MIN}}$  to  $D_{\text{MAX}}$  it is possible to determine the max  $I_{\text{RMS}}$  flowing through the input capacitor.

The use of ceramic capacitors with voltage ratings in the range of 1.5 times the maximum output voltage is recommended.

**2.3 Output capacitor**

The output capacitor is very important to satisfy the output voltage ripple requirement. Using a small inductor value is useful to reduce the size of the coil, but increases the current ripple. So, to reduce the output voltage ripple a low ESR capacitor is required. The output voltage ripple ( $V_{\text{OUT\_RIPPLE}}$ ), in continuous mode, is:

**Equation 8**

$$V_{\text{OUT\_RIPPLE}} = \Delta I \cdot \left( \text{ESR} + \frac{1}{8 \cdot C_{\text{out}} \cdot F_{\text{SW}}} \right)$$

where  $\Delta I$  is the ripple current and  $F_{\text{SW}}$  is the switching frequency.

The use of ceramic capacitors with voltage ratings in the range of 1.5 times the maximum output voltage is recommended.

**2.4 Inductor**

The inductor value is very important because it fixes the ripple current flowing through the output capacitor. The ripple current is usually fixed at 20-40% of  $I_{\text{out\_max}}$ , that is 0.1-0.2 A with  $I_{\text{out\_max}} = 0.5$  A. The inductor value is approximately obtained by the following formula:

**Equation 9**

$$L = \frac{V_{\text{in}} - V_{\text{out}}}{\Delta I} \cdot T_{\text{on}}$$

where  $T_{\text{on}}$  is the ON time of the internal switch, given by  $D \cdot T$ . The peak current through the inductor is given by:

**Equation 10**

$$I_{\text{PK}} = I_{\text{out}} + \frac{\Delta I}{2}$$

And it can be seen that if the inductor value decreases, the peak current (that has to be lower than the current limit of the device) increases. So, for fixed peak current protection, a higher value of the inductor permits a higher value for the output current.

## 2.5 Layout considerations


Due to the high switching frequency and peak current, the layout is an important design step for all switching power supplies. If the layout is not carefully done, important parameters such as efficiency and output voltage ripple could be compromised.

Short, wide traces must be implemented for main current and for power ground paths as shown in bold in *Figure 16*. The input capacitors must be placed as close as possible to the device pins as well as the inductors and output capacitors.

A common ground node minimizes ground noise, as shown in *Figure 16*.

HV pin must be floating or connected to GND and the exposed pad of the package must be connected to GND.

**Figure 16. Layout considerations**

 

### 3 Thermal considerations

The dissipated power of the device is determined by three different factors:

- Switch losses due to the nonnegligible  $R_{DS(on)}$ . These are equal to:

#### Equation 11

$$P_{ONP} = R_{DS(on)P} \cdot I_{out}^2 \cdot D$$

and

#### Equation 12

$$P_{ONN} = R_{DS(on)N} \cdot I_{out}^2 \cdot (1-D)$$

where D is the duty cycle of the application.

*Note: The duty cycle is theoretically given by the ratio between  $V_{out}$  and  $V_{in}$ , but in practice is quite higher than this value in order to compensate the losses of the overall application. Due to this reason, the switch losses related to the  $R_{DS(on)}$  increase compared to the ideal case.*

- On and Off switching losses. These are given by the following relationship:

#### Equation 13

$$P_{SW} = V_{in} \cdot I_{out} \cdot \frac{(T_{on} + T_{off})}{2} \cdot F_{SW} = V_{in} \cdot I_{out} \cdot T_{SW} \cdot F_{SW}$$

where  $T_{ON}$  and  $T_{OFF}$  are the overlap times of the voltage across the power switch and the current flowing into it during the turn-on and turn-off phases.  $T_{SW}$  is the equivalent switching time.

- Quiescent current losses:

#### Equation 14

$$P_Q = V_{in} \cdot I_Q$$

where  $I_Q$  is the quiescent current.

The overall losses are:

#### Equation 15

For channel 1

$$P_{CH1} = R_{DS(on)P1} \cdot I_{out1}^2 \cdot D_1 + R_{DS(on)N1} \cdot I_{out1}^2 \cdot (1 - D_1) + V_{in} \cdot I_{out1} \cdot T_{SW1} \cdot F_{SW1}$$

#### Equation 16

For channel 2

$$P_{CH2} = R_{DS(on)P2} \cdot I_{out2}^2 \cdot D_2 + R_{DS(on)N2} \cdot I_{out2}^2 \cdot (1 - D_2) + V_{in} \cdot I_{out2} \cdot T_{SW2} \cdot F_{SW2}$$

#### Equation 17

$$P_{TOT} = P_{CH1} + P_{CH2} + V_{in} \cdot I_Q$$

The junction temperature of device is:

**Equation 18**

$$T_J = T_A + R_{th_{J-A}} \cdot P_{TOT}$$

where  $T_A$  is the ambient temperature and  $R_{th_{J-A}}$  is the thermal resistance junction to ambient.

## 4 Demonstration board usage recommendation

The demonstration board shown in *Figure 17* is provided with a Kelvin connection which means that for each pin there are two lines available, one used to supply or sink current and the other one used to perform the needed measurement.

**Figure 17. Demonstration board layout**

 




Figure 18. Demonstration board - top layer


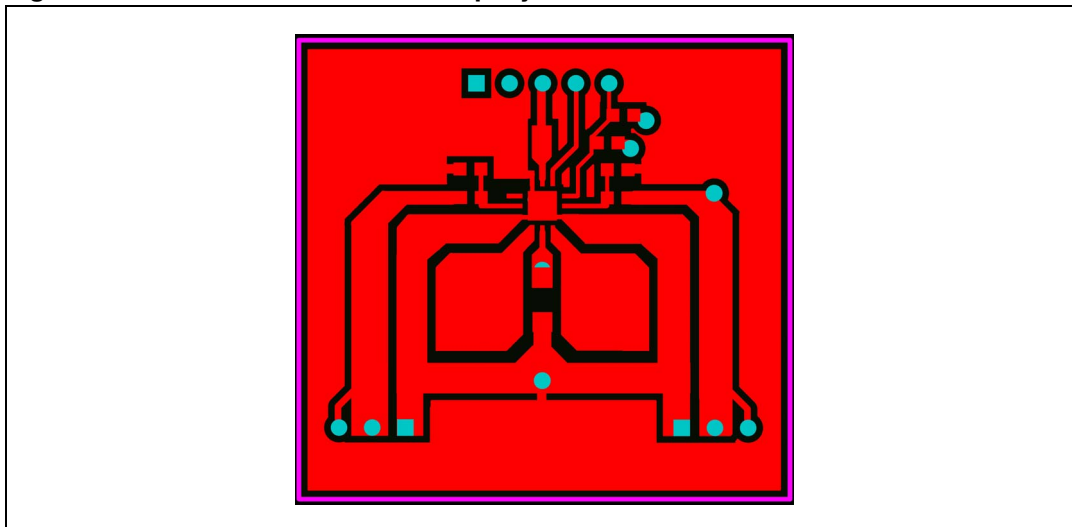


Figure 19. Demonstration board - bottom layer

 


The board has one inhibit pin available which is located on the top side of the board. This pin can be used to supply the inhibit pin with an external voltage higher than 1.3 V to turn on, or lower than 0.4 V to turn off the device.


### 4.1 External component selection

Figure 19 and 20 show the demonstration board schematic.

**Figure 20. Demonstration board schematic for ST2S06A/D**

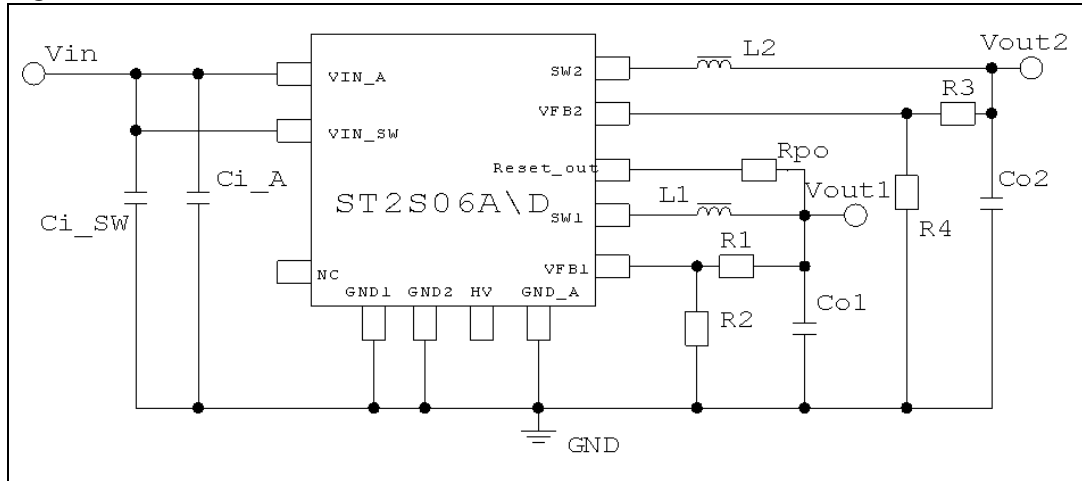

**Figure 21. Demonstration board schematic for ST2S06B**

 

In order to obtain the needed output voltage, the resistor divider must be selected in accordance with the following formula:

**Equation 19**

$$V_{OUT1,2} = V_{FB1,2} \left[ 1 + \frac{R_{1,3}}{R_{2,4}} \right]$$

with  $V_{FB1,2} = 0.8 \text{ V}$

**Table 1. Recommended resistor divider**

$V_{OUT1,2}$	$R_{1,3}$	$R_{2,4}$
1.2 V	27 kΩ	47 kΩ
3.3 V	47 kΩ	15 kΩ

The resistors dividers in [Table 1](#) are a good compromise in terms of current consumption and minimum output voltage.

*Note: If ST2S06A33 or ST2S06D33 are mounted in the demonstration board, R1 is replaced with a short-circuit and R2 is not used.*

#### 4.1.1 Capacitors selection

It is possible to use any X5R or X7R ceramic capacitor

- $C_{i\_A} = C_{i\_SW} = 4.7 \mu\text{F}$  (ceramic) or higher.
- $C_{o1} = C_{o2} = 22 \mu\text{F}$  (ceramic) or higher. It is possible to put several capacitors in parallel in order to reduce the equivalent series resistance and improve the ripple present in the output voltage.

#### 4.1.2 Inductor selection

Due to the high frequency (1.5 MHz) it is possible to use very small inductors values. In our board the device was tested with inductors in the range of  $1 \mu\text{H}$  to  $10 \mu\text{H}$ , with very good efficiency performances (see below plot in [Figure 22](#)).

As the device is able to provide an operative output current of 0.5 A, the use of inductors capable of managing at least 1.5 A is strongly recommended.

**Figure 22. Efficiency vs. output current**

 


Figure 23. Efficiency vs. inductor


 


Figure 24. Efficiency vs. output voltage

 

Note: All efficiencies are relative to one channel, the other channel is at no-load.

## 5 Bill of materials

**Table 2. BOM with most common components**

Name	Value	Material	Manufacturer	P/N
Ci_A	4.7 $\mu$ F	Ceramic	Murata	GRM21BR61E475KA12B
		Ceramic	TDK	C3216X7R1C475K
Ci_SW	4.7 $\mu$ F	Ceramic	Murata	GRM21BR61E475KA12B
		Ceramic	TDK	C3216X7R1C475K
Co1	22 $\mu$ F	Ceramic	Murata	GRM32ER61E226KE15B
		Ceramic	TDK	C3225X7R1C226M
Co2	22 $\mu$ F	Ceramic	Murata	GRM32ER61E226KE15B
		Ceramic	TDK	C3225X7R1C226M
L1	3.3 $\mu$ H		TDK	RLF7030T-3R3M4R1
			Murata	LQH66SN3R3M03L
			Coiltronics	DR73-3R3
L2	3.3 $\mu$ H		TDK	RLF7030T-3R3M4R1
			Murata	LQH66SN3R3M03L
			Coiltronics	DR73-3R3
Rpi/Rpo	120 k $\Omega$			



**Please Read Carefully:**

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2008 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)

